


Project 1

4-bit Successive Approximation A to D Converter

Major elements:

- Sample/hold amplifier (S/H)
- D/A converter
- Comparator (Schmitt trigger recommended)
- Storage register
- Clock
- Control and sequencing logic

Project 1

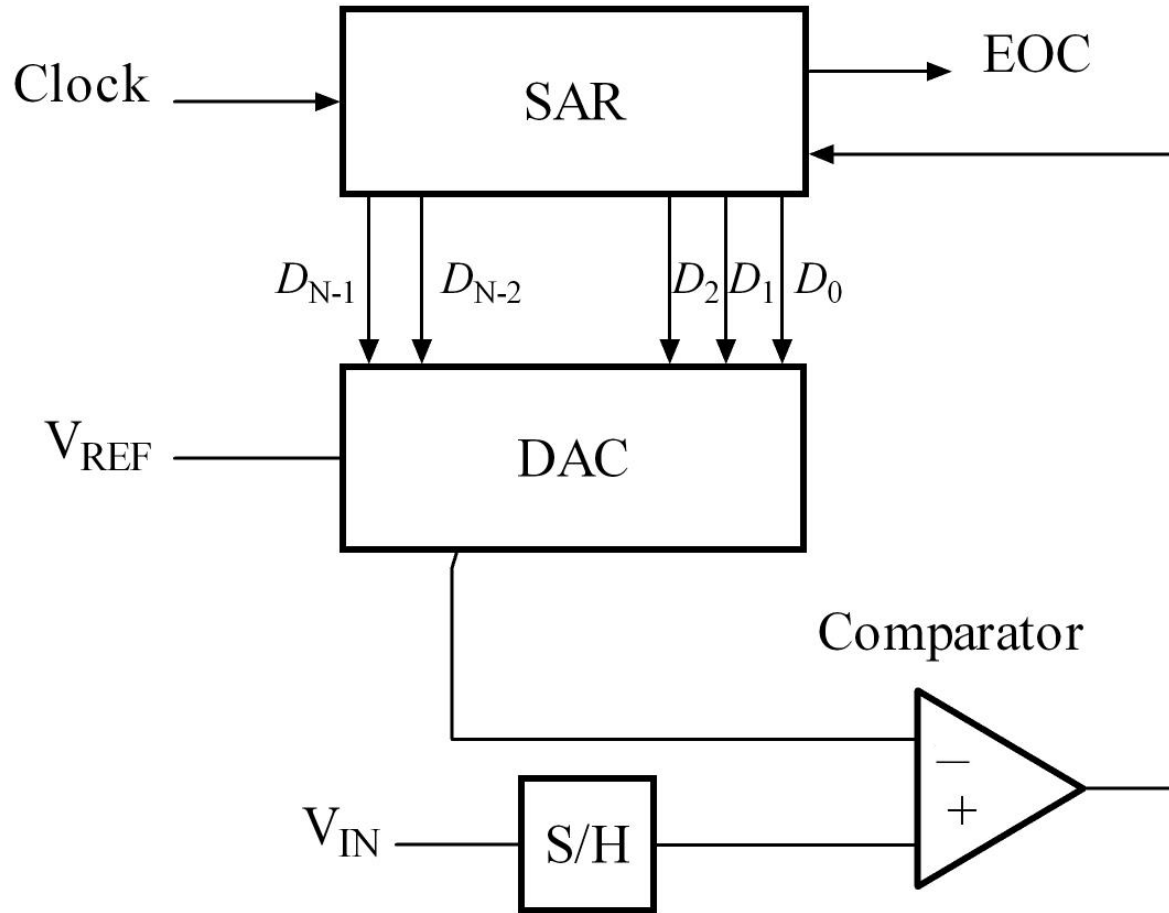

Initial Specifications: Project #1

Create a 4-bit unipolar input SAR A/D converter which will

- (1) Initiate a conversion sequence on command
- (2) Present a digital parallel 4-bit conversion result (nibble) when data ready.

Initial Specifications: Project #1

3. Have an input range of 0-5 VDC.
4. Have a data conversion of at least 100 samples/second (sps). Conversion rate in excess of 1 ksps is desired.
5. No missing codes.

Initial Specifications: Project #1


- (6) Have a unipolar power source or bipolar supply connections from bench power supply.
- (7) Have an adequate associated test plan in which all tests pass.

Your design must not use any modern processors with the following exceptions:

- Act as control for your AD converter.
- to transfer data and display the result.

Anything that is part of the 4000-series CMOS family or equivalent is fair game. You have a budget of \$100 for parts that cannot be found in the part store.

A few notes on A/D converters

- Convert an analog voltage into a digital representation
 - e.g., 2.45v  0110
 - This conversion is dependent on the range of voltages to be converted and the number of bits used to represent the voltage

Notes on A/D Converters

Resolution: the smallest possible change that can be identified (resolved). Also called Least Significant Bit (LSB).

The term “LSB” or “counts” is used in several different ways. For example, a signal may have “five counts of noise.” This means the observed noise is equivalent to five times the value of the LSB.

Notes on A/D Converters

Bits of resolution	Number distinct values	Theoretical resolution
4	16	6.25%
8	256	0.39% = 3906 ppm
10	1024	977 ppm
12	4096	244 ppm
14	16384	61 ppm
16	65536	15 ppm
20	1048576	1 ppm

Notes on A/D Converters

Resolution and reference voltage are related, because sampled signal values are interpreted as a binary fraction of the reference voltage.

If $V_{\text{ref}} = 5.00 \text{ V}_{\text{DC}}$ and we are doing an 8-bit conversion,

$$\text{Resolution} = 5\text{V}/(256 \text{ values}) = 19.5 \text{ mV/value}$$

Notes on A/D Converters

If $V_{\text{ref}} = 4.096 V_{\text{DC}}$ and we are doing a 12-bit conversion,

$$\text{Resolution} = 4.096\text{V} / (4096 \text{ values}) = 1\text{mV/value}$$

The digitized signal value is equal to the number of counts (binary value) multiplied by the resolution. Any error from the original signal is called digitization noise.

Notes on A/D Converters

